

$\vec{w}_1$   $\vec{w}_2$   $\vec{w}_3$

02/16

- Packets don't accumulate at routers

- Node-Edge Incidence matrix shows topology of graph

- valid flow rates in nullspace of incidence matrix

$$G\vec{w}_1 = \vec{0}$$


- However,  $\vec{w}_1$ ,  $\vec{w}_2$ , and  $\vec{w}_3$  are

$$G\vec{w}_2 = \vec{0}$$


closed loops that go through node 2.

$$G\vec{w}_3 = \vec{0}$$

- These are independent loops!

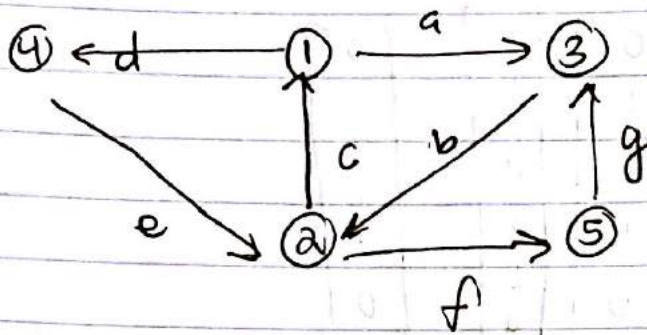

loops:

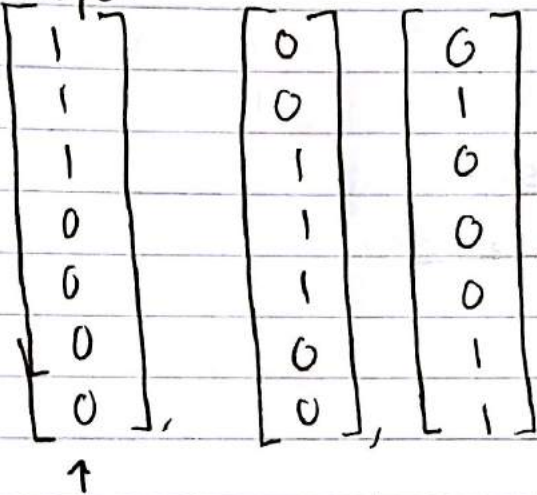


adding columns of incidence matrix  $\Rightarrow$  sums to 0.

Euler's formula:


$$\# \text{ nodes} - \# \text{ edges} + \# \text{ ind. loops} = 1.$$

If remove c, e, g, we're left w/a graph with no cycles  $\Rightarrow$  the graph is a tree.

irrorsound ideal channel

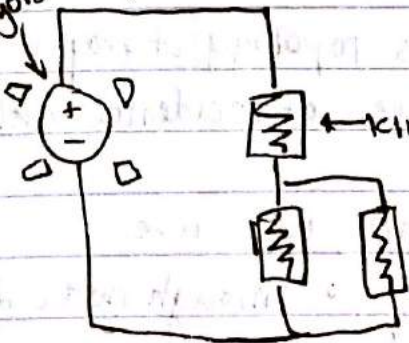


$$AV = I \cdot R$$

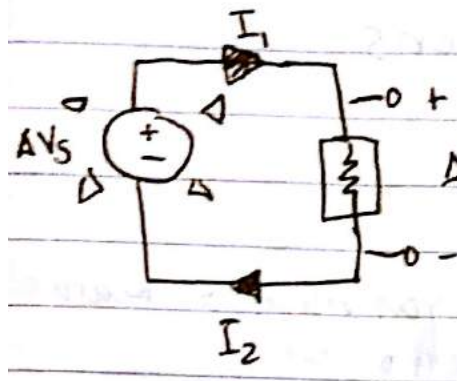

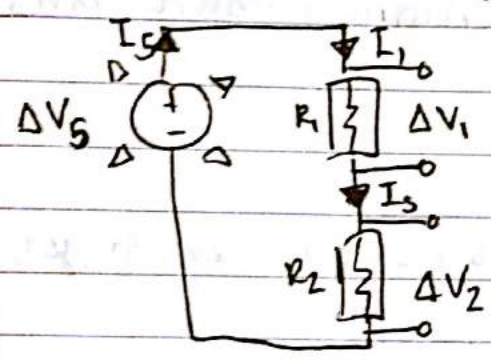- (1)  $I_1 = I_2$
- (2)  $\Delta V_0 = \Delta V_R$
- (3)  $\Delta V = I \cdot R$

When you go through kinked road, vigor is lost.



Assume  $I_S = NI$  ↳ also eqn.  
 $\hookrightarrow 100 \text{imps/sec}$


$$\Delta V_S = \Delta V_1 + \Delta V_2$$

$$I_S = I_1, I_S = I_2$$

$$\Delta V_1 = I_1 R_1$$

$$\Delta V_2 = I_2 R_2$$

1	0	0	0	0	0	=	$I_S$	$NI$
0	0	0	1	-1	-1		$I_1$	0
1	0	0	0	0	0		$I_2$	0
1	0	0	0	0	0		$\Delta V_S$	0
0	-R_1	0	0	1	0		$\Delta V_1$	0
0	0	-R_2	0	0	1		$\Delta V_2$	0

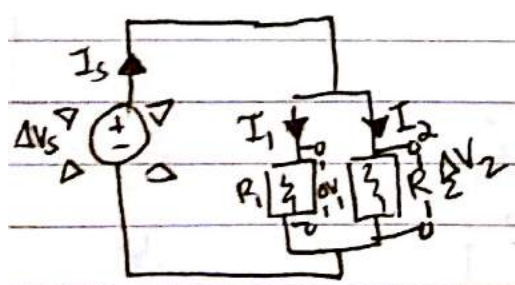

$$I_S = NI$$

$$I_1 + I_2 = I_S$$

$$\Delta V_1 = I_1 R_1$$

$$\Delta V_2 = I_2 R_2$$

$$\Delta V_1 = \Delta V_S$$

$$\Delta V_2 = \Delta V_S$$