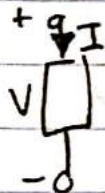


Power  $\equiv \frac{\text{Energy}}{\text{time}}$

Power =  $V \cdot I$   
 (dissipated) when  $V, I$  are (+)






Power =  $VI$   
 $V = IR$

substituting,  
 Power =  $IR \cdot I$   
 $= I^2 R$

Power =  $V \cdot \frac{V}{R}$   
 $= \frac{V^2}{R}$

Equivalence

Recall touchscreen:

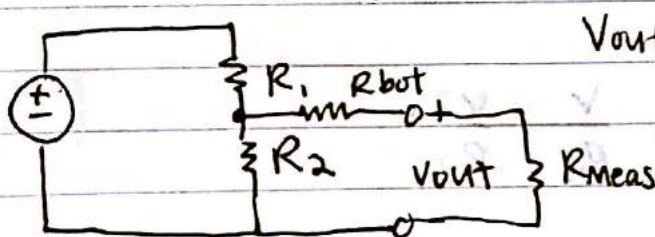


$V_{out} = \frac{R_2 \cdot 5V}{R_1 + R_2}$  "voltage divider"

$= \frac{R_2}{R_{TOT}} \cdot 5V$


-bad, because circuit is not closed w/  $R_{meas}$ .

Thevenin's Theorem:

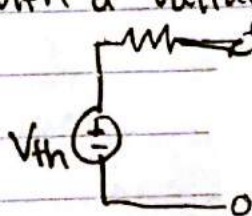A circuit made up of "linear" components, can be replaced with a voltage source and resistor.




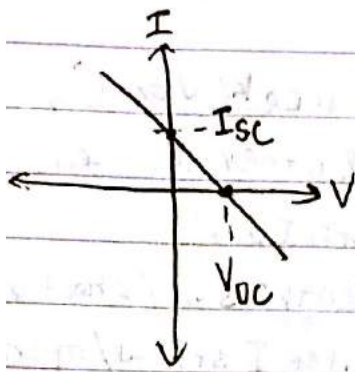(i.e. any circuit can be reduced to a dimension of 2)




because the component is linear, it can be represented as a line.

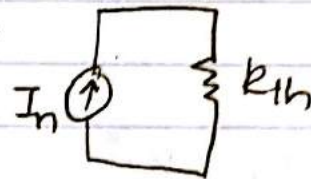Norton: A circuit can be reduced to current source + resistor.



$$V_{th} = V_{oc}$$

$$R_{th} = \frac{V_{th}}{I_{sc}}$$

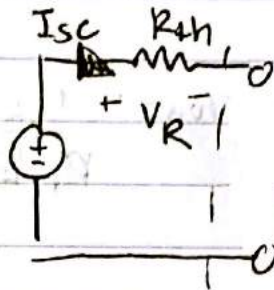


$$V_R = V_{th}$$


$$I = V/R$$

$$\rightarrow I_{sc} = V_{th} / R_{th}$$

Thevenin equivalent:

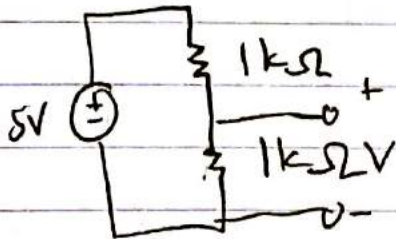

⇒

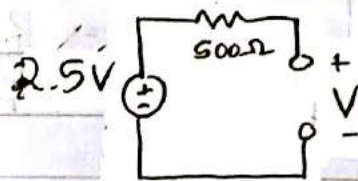

$$V_{oc} = 2.5V$$

$$I_{sc} = 0.005A$$


$$R_{th} = \frac{V_{th}}{I_{sc}} = 500\Omega$$

Superposition


$$y = ax_1 + ax_2$$

$$y = a(x_1 + x_2)$$


$$= ax_1 + ax_2$$

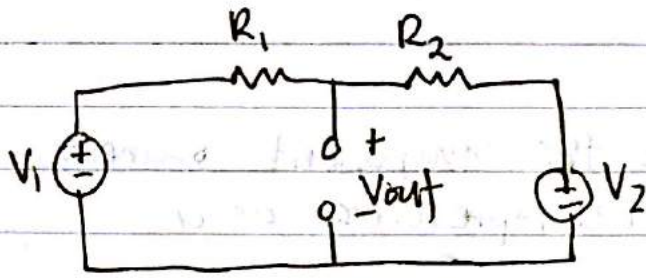

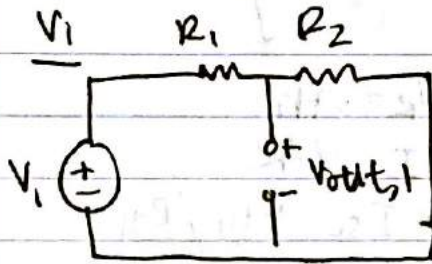For each source  $k$  (V or I),  
 \* take all other sources, set them to 0.  
 (replace other V-src w/ short)  
 (replace other I-src w/ open)  
 → compute  $V_{out,k}$  due to that source ( $k$ ).  
 \* sum up  $V_{out,k}$  for all  $k$ .


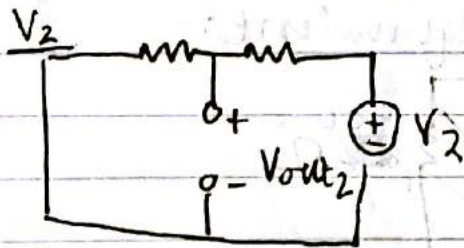
$$V_{out1} = \frac{R_2}{R_1 + R_2} \cdot V_1$$





$$V_{out2} = \frac{R_1}{R_1 + R_2} \cdot V_2$$

$$V_{out} = \frac{R_1 V_2 + R_2 V_1}{R_1 + R_2}$$

If  $R_1 = R_2$ ,

$$V_{out} = \frac{V_1 + V_2}{2}$$

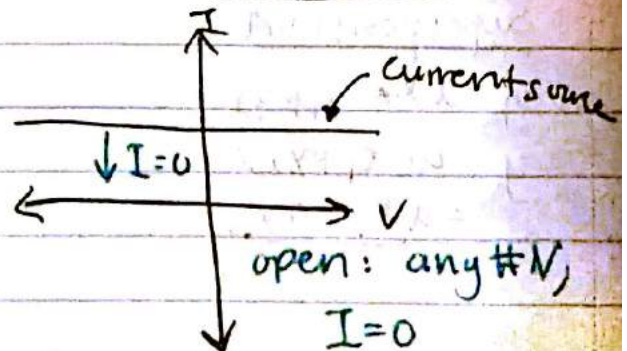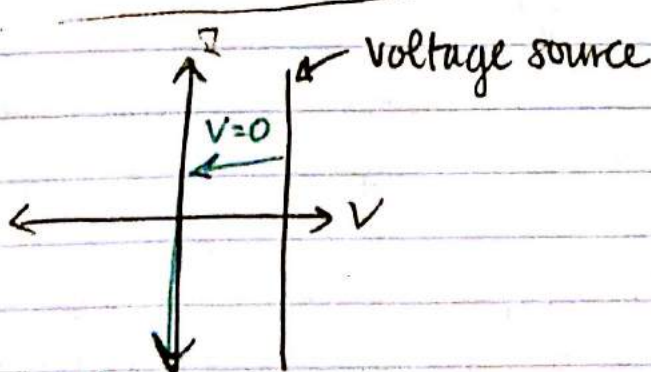

ideal wire: any # current,  $\Delta V = 0$

