
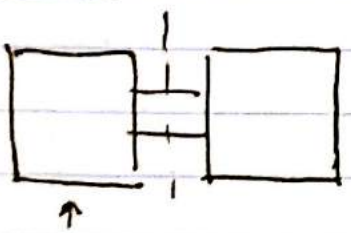


Theremin

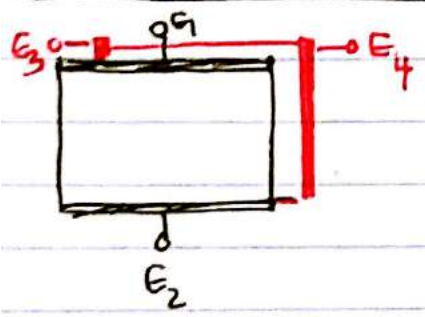


can transform to find equivalent



2D-Resistive Touchscreen



Measure x-pos:

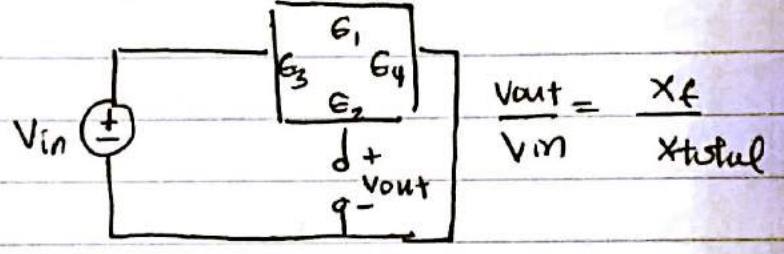

Measure y-pos:

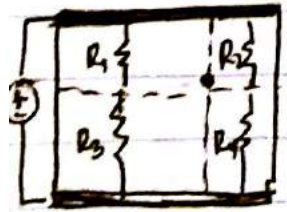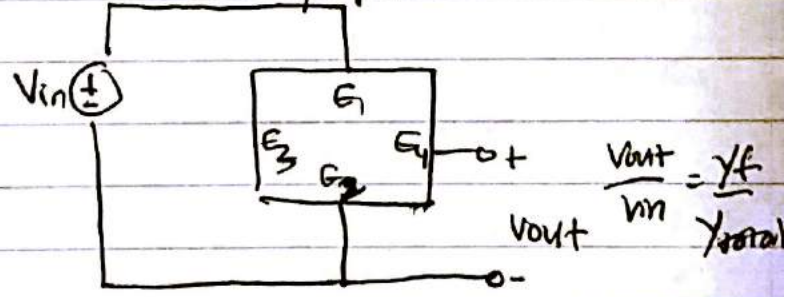

$$\frac{R_1}{R_3} = \frac{R_2}{R_4}$$


(BVT)

$R_1 \neq R_2$  b/c cross-sectional area

Multitouch

R-screen: analog voltage  $\leftrightarrow$  touch coordinates

A screen?


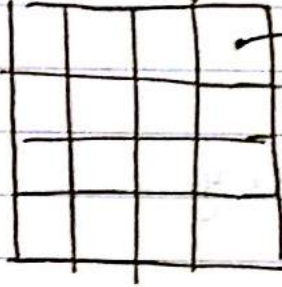


is their finger above me or not?

### The Capacitor

- Capacitance can change w/ presence of paper.

Basics:  $q + v$

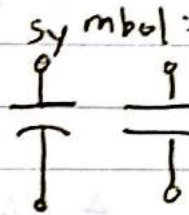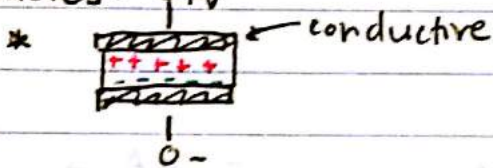

parallel plate capacitor

\* Capacitance:  $\frac{\text{Charge stored}}{V \text{ across}}$

$$Q = C \cdot V$$

C capacitance

$C \equiv Q / V$  Farads (F)  
"buckets of charge"


\* Calculating capacitance:

→ dimensions


→ material parameters

$$C = \epsilon \cdot A$$

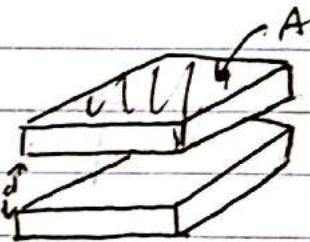
$\epsilon$  ← permittivity  
 $A$  ← cross-sectional area



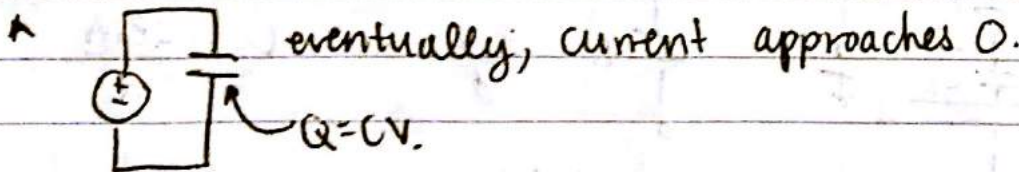air:  $\epsilon = 8.85 \cdot 10^{-12} \text{ F/m}$ .




$$I = C \cdot \frac{dV}{dt}$$

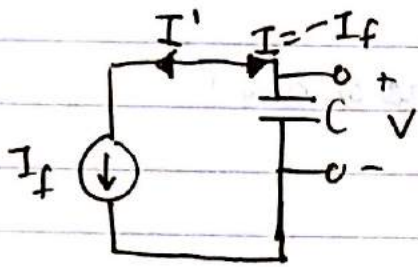


$$I = C \frac{dV}{dt}$$

→ voltage decreasing

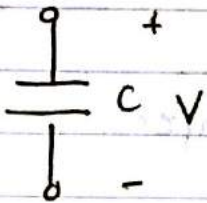

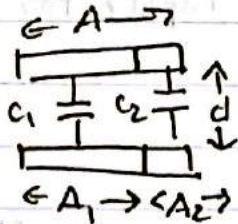There is energy stored in the capacitor  
 $E = \frac{1}{2} CV^2$  ( $E = CV^2$ )




$$A_1 + A_2 = A \quad C_{\text{orig}} = \frac{\epsilon A}{d}$$

$$C_1 = \frac{\epsilon A_1}{d} \quad C_2 = \frac{\epsilon A_2}{d}$$


$C_{\text{orig}} = C_1 + C_2$  in parallel.

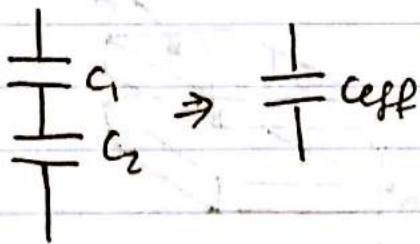$C_{\text{eff}} = C_1 + C_2 + \dots$  for parallel capacitors



$$C_{\text{eff}}^{-1} = \frac{1}{C_1} + \frac{1}{C_2}$$
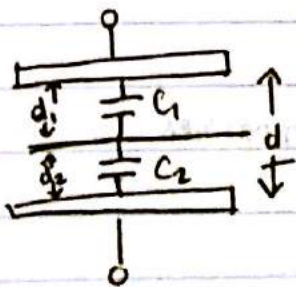
$$= \frac{C_1 C_2}{C_1 + C_2} = C_1 \parallel C_2$$



$$\frac{1}{C} = \frac{\epsilon A}{d}$$

$$C_1 = \frac{\epsilon A}{d_1}$$

$$= \frac{\epsilon A}{d_1 + d_2}$$

$$C_2 = \frac{\epsilon A}{d_2}$$

$$C^{-1} = \frac{d_1 + d_2}{\epsilon A} = \frac{1}{C_1} + \frac{1}{C_2} \quad \text{!!!}$$