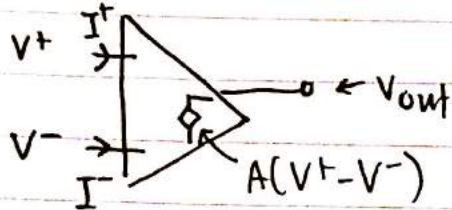


Op-Amps


Golden Rules Review:



① $I^+ = I^- = 0$.


② $V^+ = V^-$ (1) why?

(2) when?

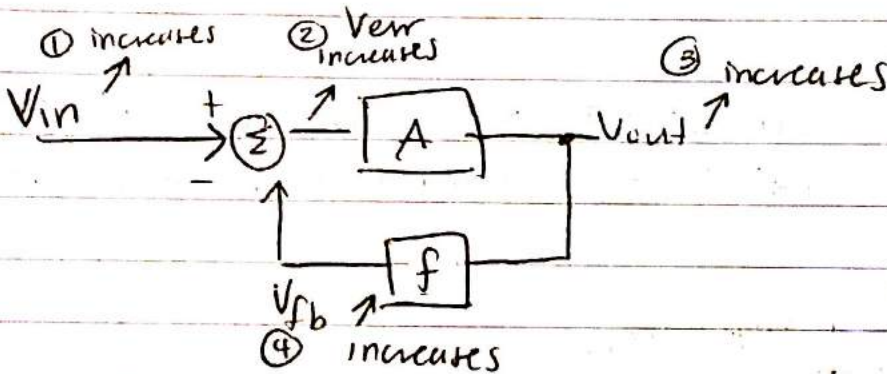

but in the next cycle, V_{err} decreases, ($V_{fb} + V_{err} = V_{in}$)
 V_{out} decreases

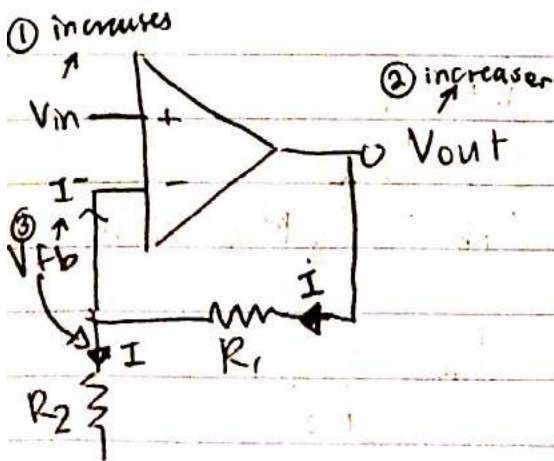pos/neg. feedback dependent on Σ
 neg if -
 pos if +




V_{fb} increases - because $I^- = 0$.


$$V_{fb} = \frac{R_2}{R_1 + R_2} \cdot V_{out}, \quad f = \frac{R_2}{R_1 + R_2}$$

Since $V^- \uparrow$, $V_{out} \downarrow$.

What would happen if :

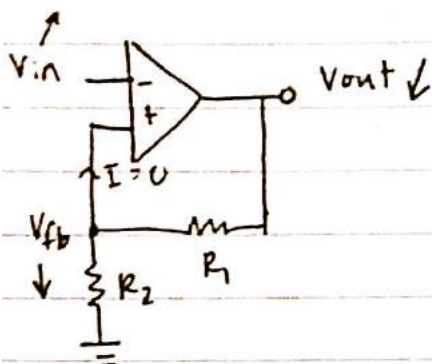

pos. feedback - slams to 0.

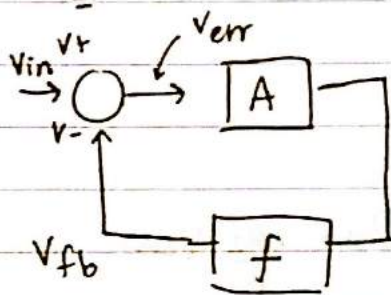

$$V_{err} = V^+ - V^-$$

$$V_{out} = A \cdot V_{err}$$

$$V^- = V_{fb} = f \cdot V_{out}$$

$$V_{out} = A (V^+ - f V_{out})$$

$$\rightarrow V_{out} = \frac{A \cdot V^+}{1 + Af}$$


$$V_{fb} = f \cdot \frac{A V^+}{1 + Af} = V^-$$

$$\text{If } A \rightarrow \infty, V_{fb} \rightarrow V^+$$

$$\text{So } V_{fb} = V^- = V^+$$

Also,

$$V_{int} = \frac{V^+}{f}$$

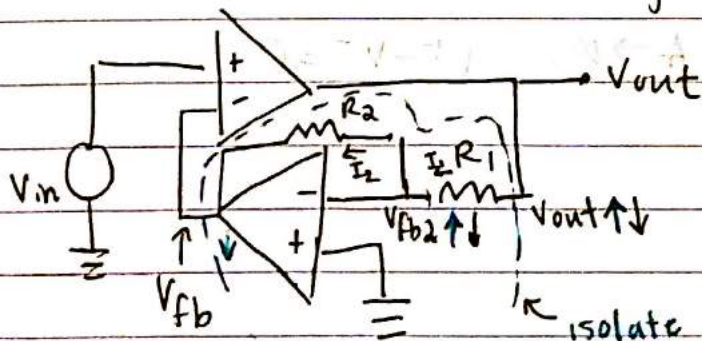


$$V_{fb2} = 0 \quad (V^+ = 0)$$


$$I_1 = \frac{V_{out}}{R_1}$$

$$\frac{-R_2}{R_1} V_{out} \text{ because } V_{fb2} = 0$$
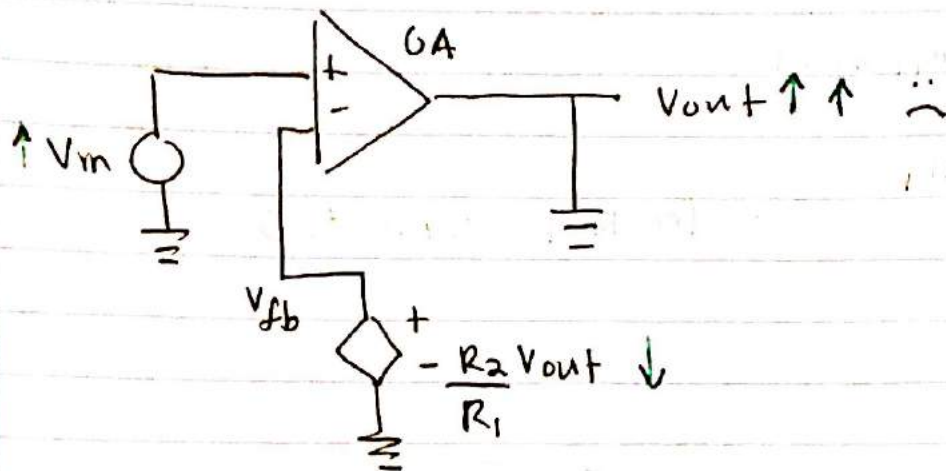
$$\text{So } V_{fb} = \frac{-R_2}{R_1} V_{out}$$




So we switch $+/-$.

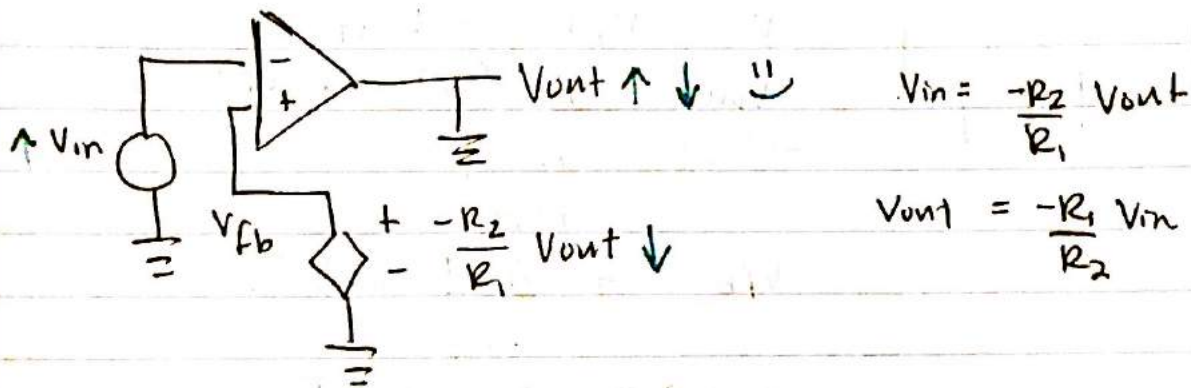

$$V^- = \frac{fA}{1 + Af} V^+$$
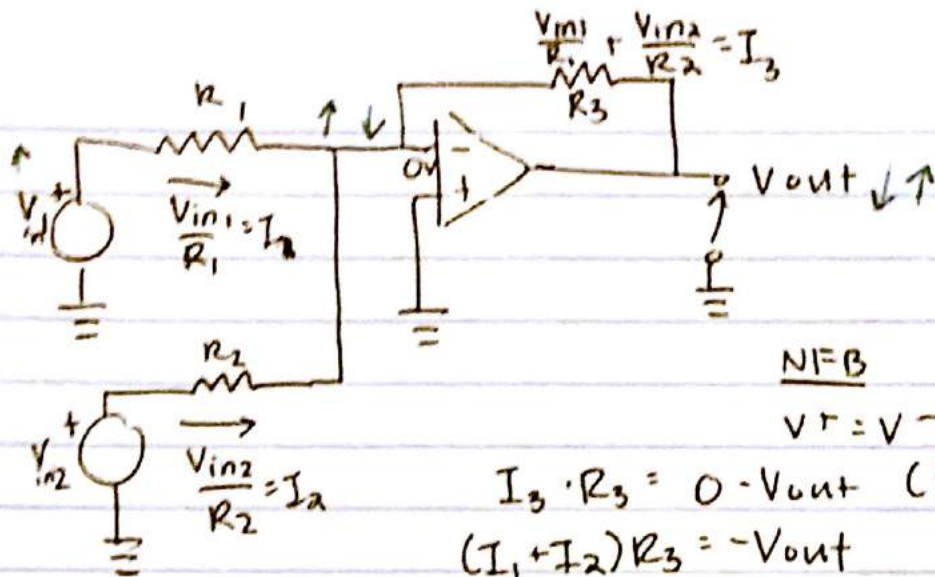
$$V^+ - V^- = \frac{1}{1 + Af} V^+ \quad \text{IF } A \rightarrow \infty, \quad V^+ - V^- = 0$$



$N=B$

$V^+ = V^-$

$$I_3 \cdot R_3 = 0 - V_{out} \text{ (KVL)}$$

$$(I_1 + I_2) R_3 = -V_{out}$$

$$V_{out} = -\left(\frac{V_{in1}}{R_1} + \frac{V_{in2}}{R_2}\right) R_3$$

$$V_{out} = -V_{in1} \left(\frac{R_3}{R_1}\right) - V_{in2} \left(\frac{R_3}{R_2}\right)$$