

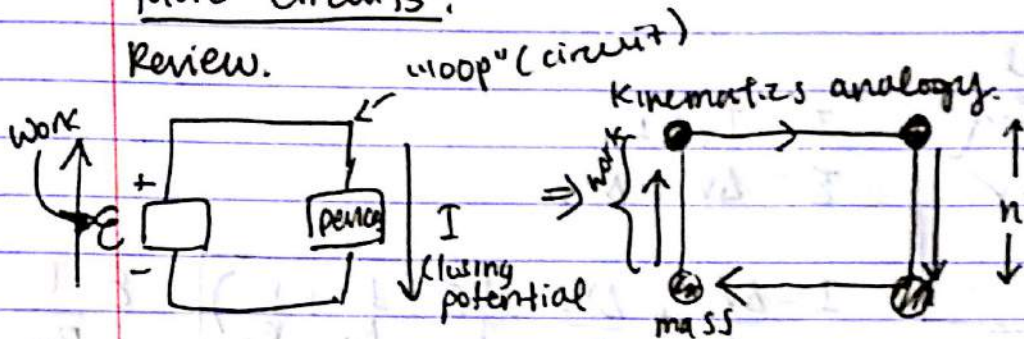


More Circuits!

Review.

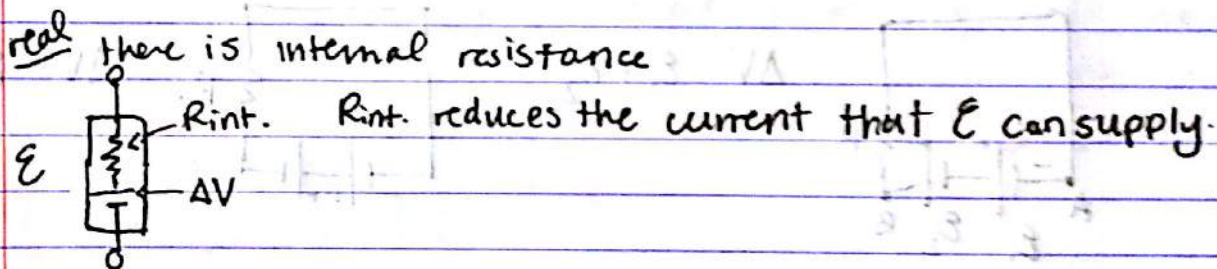


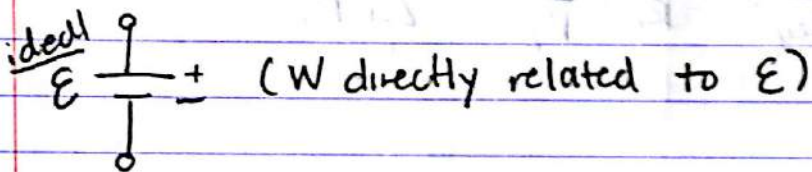\mathcal{E} = electromotive force = work per unit charge = ΔV




Series

ΔV shared

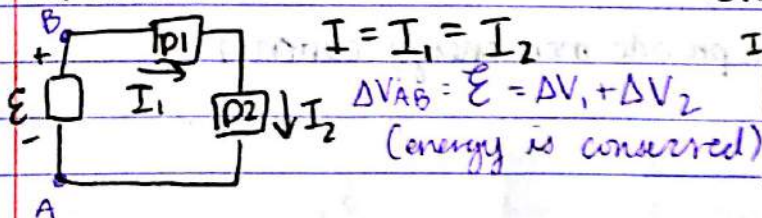


Parallel

charge (I) shared

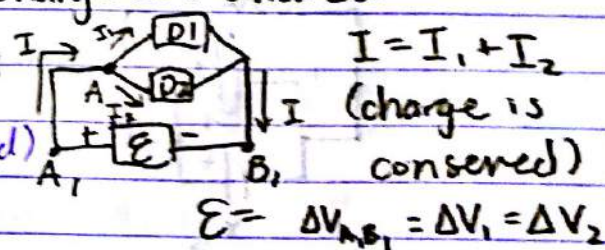


R-Series

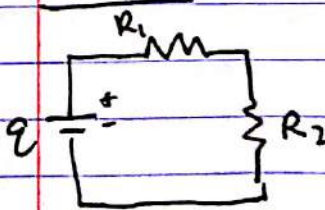


$$I = I_1 = I_2$$

$$\mathcal{E} = \Delta V_1 + \Delta V_2 = I_1 R_1 + I_2 R_2$$
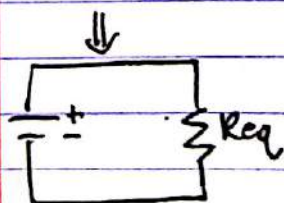
$$\boxed{\mathcal{E} = I(R_1 + R_2)} = I R_{eq}, \quad R_{eq} = R_1 + R_2 = \sum_{i=1}^n R_i$$



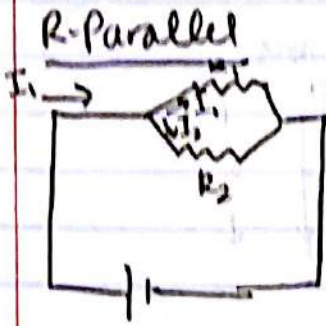


$$I = I_1 + I_2$$

$$\mathcal{E} = \Delta V_1 = \Delta V_2$$


$$I = \frac{\Delta V_1}{R_1} + \frac{\Delta V_2}{R_2} = \boxed{\mathcal{E} \left(\frac{1}{R_1} + \frac{1}{R_2} \right)} = \mathcal{E} \frac{1}{R_{eq}}$$

$$\therefore \frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} = \sum_i \frac{1}{R_i}$$

\mathcal{E}-Series

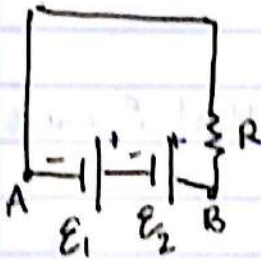

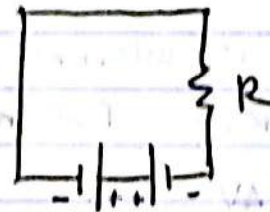
$$\Delta V = \mathcal{E}_1 + \mathcal{E}_2$$





$$\Delta V = \mathcal{E}_1 - \mathcal{E}_2$$

\mathcal{E}-Parallel

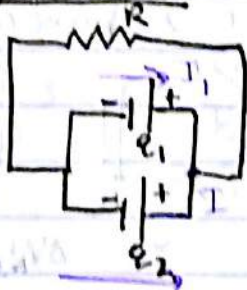

(can provide more energy-current)

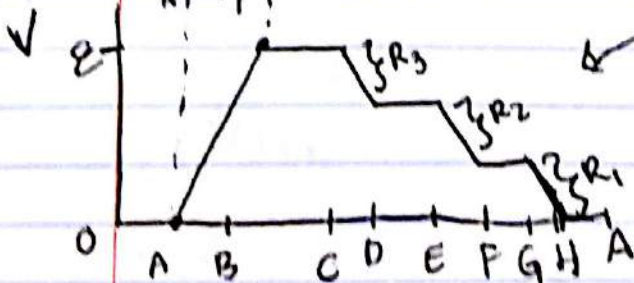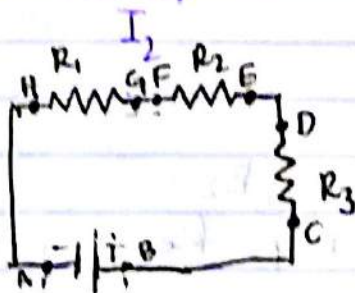


So energy is conserved.

Kirchhoff's Loop Law (Rule 2)

1) Charge is conserved ($I = I_1 + I_2 + \dots$)

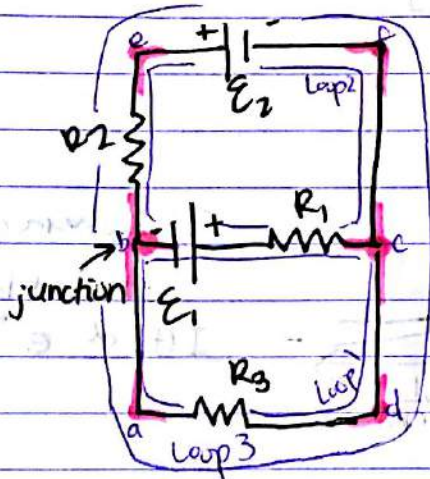2) Energy is conserved ($\Delta V = \Delta V_1 + \Delta V_2 + \dots$)



Charge is conserved @ a Junction
Energy is conserved @ a Loop

- junctions w/ lots of wires are helpful. (b & c)


- choose small loops (ex. aefda doesn't help much.)

$$\text{Junction: } \sum_{i \text{ junction}} I_{i \text{ in}} = \sum_{i \text{ junction}} I_{i \text{ out}}$$

$$\text{Loop: } \sum_{i \text{ loop}} \Delta V_i = 0$$

must be closed loop.

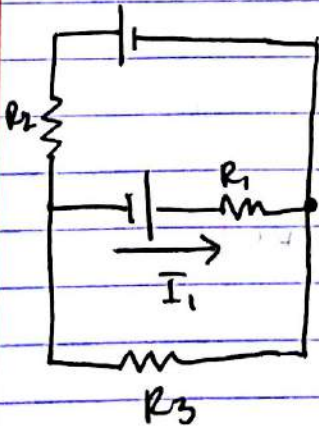- decide on direction of travel (clockwise)



*these directions are assumptions - stay consistent




- correct for direction based on $I > 0$ or $I < 0$.

@ Junction C
 $I_1 + I_2 = I_3$

@ Loop abcda
 $\epsilon_1 - R_1 I_1 - R_3 I_3 = 0$

@ Loop befcb
 $\epsilon_2 + R_1 I_1 - \epsilon_1 - I_2 R_2 = 0$
↑
against direction of I_1

RC Circuit

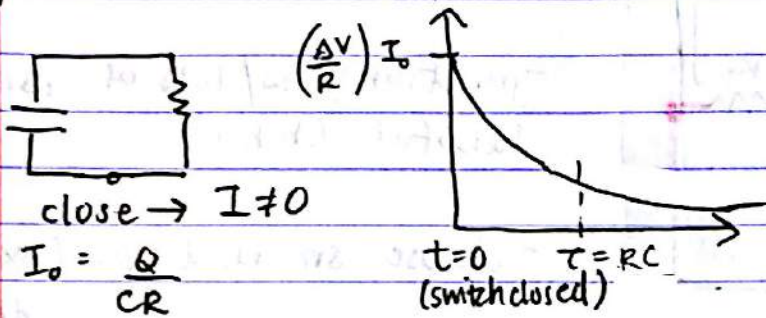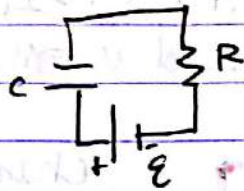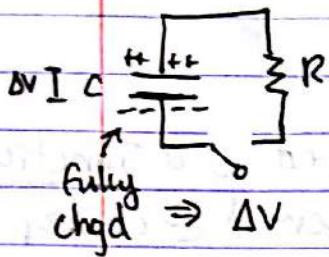

$$\Delta V - IR = 0$$

$$\frac{Q}{C} - IR = 0$$

$$\frac{Q}{C} + \frac{dQ}{dt} R = 0$$

$$-R \frac{dQ}{dt} = \frac{Q}{C}$$

$$\int_{Q_0}^Q \frac{dQ}{Q} = \int_0^t \frac{dt}{RC} = \ln \frac{Q}{Q_0} = \frac{-t}{RC}$$

$$\therefore Q(t) = Q_0 e^{-t/RC}$$