
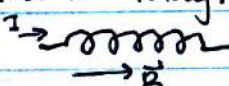




Circuits w/ Inductors

Energy stored in \vec{E} field


 $\Delta V \propto q$ energy stored = $\frac{1}{2} CV^2$
 $C = \frac{q}{\Delta V} \rightarrow \Delta V \sim \frac{1}{C}!$

Energy stored in magnetic field \vec{B}
 solenoid $\vec{I} \rightarrow$ 

How do we find ΔV ? ←

$\frac{dI}{dt} \neq 0 \rightarrow \frac{dB}{dt} \neq 0 \rightarrow \frac{d\Phi_B}{dt} \neq 0$ ← induced EMF

so $\mathcal{E}_L \propto -\frac{dI}{dt}$ self-inductance (L) is constant of proportionality.
 ↑
 opposes change.


Energy stored (U_B):

$P = \frac{dW}{dt}$ $dW = P dt$

$P = I \mathcal{E}_L = I L \frac{dI}{dt}$, $\int_0^I P dt = \int_0^I I L dI$

$\therefore \boxed{W = \frac{1}{2} LI^2 = U_B}$ ($I=0, U_B=0$)

SERIES

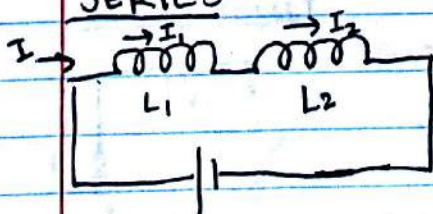


$L_1 \frac{dI}{dt} + L_2 \frac{dI}{dt} = V$ ← $L_{eff} \frac{dI}{dt}$

$\therefore \boxed{L_{eff} = L_1 + L_2}$

$I = I_1 = I_2$

Parallel

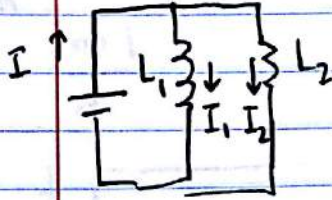
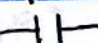



$$L_1 \frac{dI_1}{dt} = L_2 \frac{dI_2}{dt} = L_{eff} \frac{dI}{dt}$$


$$\text{and } \frac{dI}{dt} = \frac{dI_1}{dt} + \frac{dI_2}{dt}$$

$$\begin{array}{l} L_1 \frac{dI_1}{dt} = L_2 \frac{dI_2}{dt} \\ \therefore \frac{dI_1}{dt} = \frac{L_2}{L_1} \frac{dI_2}{dt} \end{array} \quad \left| \begin{array}{l} L_2 \frac{dI_2}{dt} = L_{eff} \left(\frac{dI_1}{dt} + \frac{dI_2}{dt} \right) \\ L_2 \frac{dI_2}{dt} = L_{eff} \left(\frac{L_2}{L_1} \frac{dI_2}{dt} + \frac{dI_2}{dt} \right) \\ L_2 = L_{eff} \left(\frac{L_2 + L_1}{L_1} \right) \end{array} \right.$$

$$L_{eff} = \frac{L_1 L_2}{L_2 + L_1} \quad \left| \frac{1}{L_{eff}} = \frac{1}{L_1} + \frac{1}{L_2} \right.$$

	Resistor 	Capacitor 	Inductor 
Main eq	$\Delta V = IR$	$\Delta V = q/c$	$\mathcal{E}_L = -L \frac{dI}{dt}$
Series	$R_{eq} = \sum_i R_i$	$\frac{1}{C_{eq}} = \sum_i \frac{1}{C_i}$	$I_{eq} = \sum_i L_i$
Parallel	$\frac{1}{R_{eq}} = \sum_i \frac{1}{R_i}$	$C_{eq} = \sum_i C_i$	$I_{eq} = \sum_i \frac{1}{I_i}$

RL Circuit

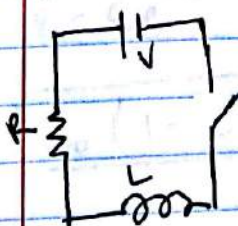


- inductors resist sudden changes by generating an opposing current.

$$t=0 \text{ switch open} \Rightarrow \frac{dI}{dt} \neq 0$$

$$t>0 \text{ switch closed}$$

$t=0$ switch open
 $t>0$ closed

RL Circuit [Cont.]

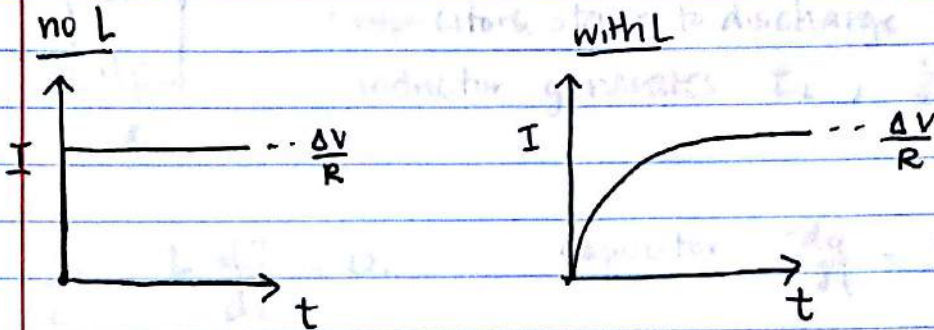


$$\mathcal{E} - IR - L \frac{dI}{dt} = 0 \quad \rightarrow \quad \mathcal{E} - IR = L \frac{dI}{dt}$$

$$\int_0^t \frac{dt}{L} = \int_0^I \frac{dI}{\mathcal{E} - IR}$$

$$\frac{1}{L} t = -\frac{1}{R} \ln(\mathcal{E} - IR) \Big|_0^I$$

$$t = -\frac{L}{R} \ln\left(\frac{\mathcal{E} - IR}{\mathcal{E}}\right)$$
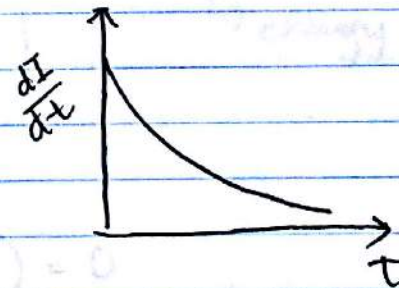
$$e^{-tR/L} = \frac{\mathcal{E} - IR}{\mathcal{E}}$$




so \mathcal{E} becomes negligible

$$\mathcal{E} e^{-tR/L} = \mathcal{E} - IR$$

$$\mathcal{E} - \mathcal{E} e^{-tR/L} = IR$$

$$\boxed{I_0 (1 - e^{-tR/L}) = I}$$

LC Circuit

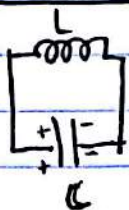

$t=0$ close switch

- capacitor starts to discharge $\rightarrow I$
- inductor generates \mathcal{E}_L , $\frac{dI}{dt} \neq 0$ b/c capacitor

$$\frac{q}{C} - L \frac{dI}{dt} = 0$$


$$\text{capacitor: } -\frac{dq}{dt} = I$$

$$\frac{q}{C} + L \frac{d^2q}{dt^2} = 0 \quad \leftarrow \text{simple harmonic motion}$$

$$\frac{q}{CL} + \frac{d^2q}{dt^2} = 0$$

$$q(t) = q_0 \cos(\omega t + \phi)$$

$$\omega = \sqrt{\frac{1}{CL}}$$

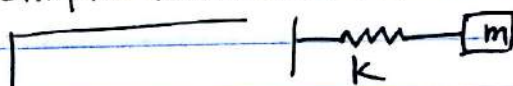

$$\frac{d^2x}{dt^2} + \frac{k}{m}x = 0, \quad x(t) = x_0 \cos(\omega t + \phi)$$

$$\omega = \sqrt{\frac{k}{m}}$$

$t=0 \rightarrow$ energy of \vec{E}
 \hookrightarrow energy of \vec{B} .

Plugging in,

$$\cos(\omega t + \phi) (-\omega^2 + \frac{1}{LC}) = 0$$

$$\text{for all } t, \text{ valid if } -\omega^2 + \frac{1}{LC} = 0. \quad // \quad \omega = \sqrt{\frac{1}{LC}}$$